

# Computer Architecture Report #1: Register File

Joanna Whittam (15319524)

Feb. 24th 2017

## 1 VHDL components

### 1.1 Reg

#### 1.1.1 Reg Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity reg is
    Port ( D: in STD_LOGIC_VECTOR (15 downto 0);
          load, CLK: in STD_LOGIC;
          Q: out STD_LOGIC_VECTOR (15 downto 0) );
end reg;

architecture Behavioral of reg is

begin
    process(CLK)
    begin
        if (rising_edge(CLK)) then
            if load='1' then
                Q <= D after 5 ns;
            end if;
        end if;
    end process;
end Behavioral;
```

#### 1.1.2 Reg Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY reg_tb IS
END reg_tb;

ARCHITECTURE behavior OF reg_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT reg
    PORT( D: IN std_logic_vector(15 downto 0);
          load, CLK: IN std_logic;
          Q: OUT std_logic_vector(15 downto 0) );
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal D: std_logic_vector(15 downto 0) := (others => '0');
```

```
signal load: std_logic := '0';
```

```
signal CLK: std_logic := '0';
```

```
--Outputs
```

```
signal Q: std_logic_vector(15 downto 0);
```

```
-- Clock period definitions
```

```
constant CLK_period: time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: reg PORT MAP (
```

```
    D => D,
```

```
    load => load,
```

```
    CLK => CLK,
```

```
    Q => Q
```

```
);
```

```
-- Clock process definitions
```

```
CLK_process :process
```

```
begin
```

```
    CLK <= '0';
```

```
    wait for CLK_period/2;
```

```
    CLK <= '1';
```

```
    wait for CLK_period/2;
```

```
end process;
```

```
-- Stimulus process
```

```
stim_proc: process
```

```
begin
```

```
    -- hold reset state for 50 ns.
```

```
    wait for 5 ns;
```

```
    D <= "0000000000001111";
```

```
    wait for CLK_period*20;
```

```
    load <= '1';
```

```
    wait for CLK_period*20;
```

```
    load <= '0';
```

```
    D <= "0000000011110000";
```

```
    wait for CLK_period*20;
```

```
    load <= '1';
```

```
    wait for CLK_period*20;
```

```
    load <= '0';
```

```
    D <= "0000111100000000";
```

```
    wait for CLK_period*20;
```

```
    load <= '1';
```

```
    wait for CLK_period*20;
```


```

        load <= '0';

        D <= "1111000000000000";
        wait for CLK_period*20;
        load <= '1';
        wait for CLK_period*20;
        load <= '0';
        wait;
    end process;
END;

```

### 1.1.3 Reg Test Results

 

## 1.2 Mux2\_16bit

In my file this entity is incorrectly named as mux2\_4bit. This will be changed in later versions of the code.

### 1.2.1 Mux2\_16bit Code

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mux2_4bit_tb IS
END mux2_4bit_tb;

ARCHITECTURE behavior OF mux2_4bit_tb IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT mux2_4bit
    PORT( S: in STD_LOGIC;
          In0, In1: in STD_LOGIC_VECTOR (15 downto 0);
          Z: out STD_LOGIC_VECTOR (15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal S : std_logic := '0';
    signal In0 : std_logic_vector(15 downto 0) := (others => '0');
    signal In1 : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal Z : std_logic_vector(15 downto 0);

BEGIN

```

```

-- Instantiate the Unit Under Test (UUT)
 uut: mux2_4bit PORT MAP (
        S => S,
        In0 => In0,
        In1 => In1,
        Z => Z
    );

-- Stimulus process
 stim_proc: process
 begin
        In0 <= "0000000000000000";
        In1 <= "1111111111111111";

        S <= '0';
        wait for 100 ns;

        S <= '1';
        wait for 100 ns;
    end process;
END;

```

### 1.2.2 Mux2\_16bit Test Bench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mux2_4bit_tb IS
END mux2_4bit_tb;

ARCHITECTURE behavior OF mux2_4bit_tb IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT mux2_4bit
    PORT(
        S: in  STD_LOGIC;
        In0, In1: in  STD_LOGIC_VECTOR (15 downto 0);
        Z: out STD_LOGIC_VECTOR (15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal S : std_logic := '0';
    signal In0 : std_logic_vector(15 downto 0) := (others => '0');
    signal In1 : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal Z : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: mux2_bit PORT MAP (
        S => S,
        In0 => In0,

```

```

        In1 => In1,
        Z => Z
    );


    -- Stimulus process
    stim_proc: process
    begin
        In0 <= "0000000000000000";
        In1 <= "1111111111111111";

        S <= '0';
        wait for 100 ns;

        S <= '1';
        wait for 100 ns;
    end process;
END;

```

### 1.2.3 Mux2\_16bit Test Results

 

## 1.3 Mux8\_16bit

### 1.3.1 Mux8\_16bit Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux8_16bit is
    Port ( S0,S1,S2: in STD_LOGIC;
          In0,In1,In2,In3,In4,In5,In6,In7: in STD_LOGIC_VECTOR (15 downto 0);
          Z: out STD_LOGIC_VECTOR (15 downto 0));
end mux8_16bit;

architecture Behavioral of mux8_16bit is
begin
    Z <= In0 after 5 ns when S2='0' and S1='0' and S0='0' else
        In1 after 5 ns when S2='0' and S1='0' and S0='1' else
        In2 after 5 ns when S2='0' and S1='1' and S0='0' else
        In3 after 5 ns when S2='0' and S1='1' and S0='1' else
        In4 after 5 ns when S2='1' and S1='0' and S0='0' else
        In5 after 5 ns when S2='1' and S1='0' and S0='1' else
        In6 after 5 ns when S2='1' and S1='1' and S0='0' else
        In7 after 5 ns when S2='1' and S1='1' and S0='1';
end Behavioral;

```

### 1.3.2 Mux8\_16bit Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mux8_16bit_tb IS
END mux8_16bit_tb;

ARCHITECTURE behavior OF mux8_16bit_tb IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT mux8_16bit
    PORT( S0,S1,S2: in STD_LOGIC;
          In0,In1,In2,In3,In4,In5,In6,In7: in STD_LOGIC_VECTOR (15 downto 0);
          Z: out STD_LOGIC_VECTOR (15 downto 0));
    END COMPONENT;

    --Inputs
    signal S0 : std_logic := '0';
    signal S1 : std_logic := '0';
    signal S2 : std_logic := '0';
    signal In0 : std_logic_vector(15 downto 0) := (others => '0');
    signal In1 : std_logic_vector(15 downto 0) := (others => '0');
    signal In2 : std_logic_vector(15 downto 0) := (others => '0');
    signal In3 : std_logic_vector(15 downto 0) := (others => '0');
    signal In4 : std_logic_vector(15 downto 0) := (others => '0');
    signal In5 : std_logic_vector(15 downto 0) := (others => '0');
    signal In6 : std_logic_vector(15 downto 0) := (others => '0');
    signal In7 : std_logic_vector(15 downto 0) := (others => '0');
    signal Z : std_logic_vector(15 downto 0) := (others => '0');

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: mux8_16bit PORT MAP (
        S0 => S0,
        S1 => S1,
        S2 => S2,
        In0 => In0,
        In1 => In1,
        In2 => In2,
        In3 => In3,
        In4 => In4,
        In5 => In5,
        In6 => In6,
        In7 => In7,
        Z => Z
    );

    -- Stimulus process
    stim_proc: process
    begin
        In0 <= "0000000000000011";
        In1 <= "0000000000001100";
        In2 <= "0000000000110000";
        In3 <= "0000000011000000";
    end process
end behavior;
```

```

In4 <= "0000001100000000";
In5 <= "0000110000000000";
In6 <= "0011000000000000";
In7 <= "1100000000000000";
wait for 100 ns;

-- 0
S0<='0'; S1<='0'; S2<='0';
wait for 100 ns;

-- 1
S0<='1'; S1<='0'; S2<='0';
wait for 100 ns;

-- 2
S0<='0'; S1<='1'; S2<='0';
wait for 100 ns;

-- 3
S0<='1'; S1<='1'; S2<='0';
wait for 100 ns;
-- 4
S0<='0'; S1<='0'; S2<='1';
wait for 100 ns;

-- 5
S0<='1'; S1<='0'; S2<='1';
wait for 100 ns;

-- 6
S0<='0'; S1<='1'; S2<='1';
wait for 100 ns;

-- 7
S0<='1'; S1<='1'; S2<='1';
wait;
end process;
END;

```

### 1.3.3 Mux8\_16bit Test Results

## 1.4 Decoder

### 1.4.1 Decoder Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity decoder_3to8 is
    Port (    A0,A1,A2: in  STD_LOGIC;
            Q0,Q1,Q2,Q3,Q4,Q5,Q6,Q7: out STD_LOGIC );
end decoder_3to8;

architecture Behavioral of decoder_3to8 is
begin
    Q0 <= ((not A2) and (not A1)    and (not A0))    after 5 ns;
    Q1 <= ((not A2) and (not A1)    and  A0)        after 5 ns;
    Q2 <= ((not A2) and  A1    and (not A0))    after 5 ns;
    Q3 <= ((not A2) and  A1    and  A0)        after 5 ns;
    Q4 <= ( A2        and (not A1)    and (not A0))    after 5 ns;
    Q5 <= ( A2        and (not A1)    and  A0)        after 5 ns;
    Q6 <= ( A2        and  A1        and (not A0))    after 5 ns;
    Q7 <= ( A2        and  A1        and  A0)        after 5 ns;
end Behavioral;
```

### 1.4.2 Decoder Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY decoder_3to8_tb IS
END decoder_3to8_tb;

ARCHITECTURE behavior OF decoder_3to8_tb IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT decoder_3to8
    PORT(
        A0,A1,A2: in  STD_LOGIC;
        Q0,Q1,Q2,Q3,Q4,Q5,Q6,Q7: out STD_LOGIC );
    END COMPONENT;

    --Inputs
    signal A0 : std_logic := '0';
    signal A1 : std_logic := '0';
    signal A2 : std_logic := '0';

    --Outputs
    signal Q0,Q1,Q2,Q3,Q4,Q5,Q6,Q7: std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: decoder_3to8 PORT MAP (
        A0 => A0,
```



```

        A1 => A1,
        A2 => A2,
        Q0 => Q0,
        Q1 => Q1,
        Q2 => Q2,
        Q3 => Q3,
        Q4 => Q4,
        Q5 => Q5,
        Q6 => Q6,
        Q7 => Q7
    );

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 10 ns;

        -- 0
        A0<='0'; A1<='0'; A2<='0';
        wait for 100 ns;

        -- 1
        A0<='1'; A1<='0'; A2<='0';
        wait for 100 ns;

        -- 2
        A0<='0'; A1<='1'; A2<='0';
        wait for 100 ns;

        -- 3
        A0<='1'; A1<='1'; A2<='0';
        wait for 100 ns;

        -- 4
        A0<='0'; A1<='0'; A2<='1';
        wait for 100 ns;

        -- 5
        A0<='1'; A1<='0'; A2<='1';
        wait for 100 ns;

        -- 6
        A0<='0'; A1<='1'; A2<='1';
        wait for 100 ns;

        -- 7
        A0<='1'; A1<='1'; A2<='1';
        wait;
    end process;
END;
```

### 1.4.3 Decoder Test Results



## 2 Register File

### 2.1 Register\_file Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity register_file is
    Port ( src_s0, src_s1, src_s2: in  STD_LOGIC;
          des_A0, des_A1, des_A2: in  STD_LOGIC;
          CLK: in  STD_LOGIC;
          data_src: in  STD_LOGIC;
          data: in  STD_LOGIC_VECTOR (15 downto 0);
          reg0, reg1, reg2, reg3: out  STD_LOGIC_VECTOR (15 downto 0)
          reg4, reg5, reg6, reg7: out  STD_LOGIC_VECTOR (15 downto 0) );
end register_file;

architecture Behavioral of register_file is

--COMPONENTS
    component decoder_3to8 is
        Port ( A0,A1,A2: in  STD_LOGIC;
              Q0,Q1,Q2,Q3,Q4,Q5,Q6,Q7: out  STD_LOGIC );
    end component;

    component mux2_4bit is
        Port ( S: in  STD_LOGIC;
              In0, In1: in  STD_LOGIC_VECTOR (15 downto 0);
              Z: out  STD_LOGIC_VECTOR (15 downto 0));
    end component;

    component mux8_16bit is
        Port ( S0,S1,S2: in  STD_LOGIC;
              In0,In1,In2,In3,In4,In5,In6,In7: in  STD_LOGIC_VECTOR (15 downto 0);
              Z: out  STD_LOGIC_VECTOR (15 downto 0));
    end component;

```

```

component reg
Port (  D: in STD_LOGIC_VECTOR (15 downto 0);
        load, CLK: in STD_LOGIC;
        Q: out STD_LOGIC_VECTOR (15 downto 0) );
end component;

--SIGNALS
signal  load_r0, load_r1, load_r2, load_r3, load_r4, load_r5, load_r6, load_r7: std_logic;
signal  reg0_q, reg1_q, reg2_q, reg3_q, reg4_q, reg5_q, reg6_q, reg7_q,
        data_src_mux_out, src_reg : std_logic_vector(15 downto 0);

begin
--PORT MAPS
--Registers
reg00: reg PORT MAP(
    D => data_src_mux_out,
    load => load_r0,
    Clk => Clk,
    Q => reg0_q );

reg01: reg PORT MAP(
    D => data_src_mux_out,
    load => load_r1,
    Clk => Clk,
    Q => reg1_q );

reg02: reg PORT MAP(
    D => data_src_mux_out,
    load => load_r2,
    Clk => Clk,
    Q => reg2_q );

reg03: reg PORT MAP(
    D => data_src_mux_out,
    load => load_r3,
    Clk => Clk,
    Q => reg3_q );

reg04: reg PORT MAP(
    D => data_src_mux_out,
    load => load_r4,
    Clk => Clk,
    Q => reg4_q );

reg05: reg PORT MAP(
    D => data_src_mux_out,
    load => load_r5,
    Clk => Clk,
    Q => reg5_q );

reg06: reg PORT MAP(
    D => data_src_mux_out,
    load => load_r6,

```

```

        Clk => Clk,
        Q => reg6_q );

reg07: reg PORT MAP(
    D => data_src_mux_out,
    load => load_r7,
    Clk => Clk,
    Q => reg7_q );

--Decoder
decoder: decoder_3to8 PORT MAP(
    A0 => des_A0,
    A1 => des_A1,
    A2 => des_A2,
    Q0 => load_r0,
    Q1 => load_r1,
    Q2 => load_r2,
    Q3 => load_r3,
    Q4 => load_r4,
    Q5 => load_r5,
    Q6 => load_r6,
    Q7 => load_r7 );

-- Multiplexers
data_src_mux2_4bit: mux2_4bit PORT MAP(
    S => data_src,
    In0 => data,
    In1 => src_reg,
    Z => data_src_mux_out);

Inst_mux8_16bit: mux8_16bit PORT MAP(
    S0 => src_s0,
    S1 => src_s1,
    S2 => src_s2,
    In0 => reg0_q,
    In1 => reg1_q,
    In2 => reg2_q,
    In3 => reg3_q,
    In4 => reg4_q,
    In5 => reg5_q,
    In6 => reg6_q,
    In7 => reg7_q,
    Z => src_reg);

reg0 <= reg0_q;
reg1 <= reg1_q;
reg2 <= reg2_q;
reg3 <= reg3_q;
reg4 <= reg4_q;
reg5 <= reg5_q;
reg6 <= reg6_q;
reg7 <= reg7_q;
end Behavioral;

```

## 2.2 Register\_file Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY register_file_tb IS
END register_file_tb;

ARCHITECTURE behavior OF register_file_tb IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT register_file
    PORT(
        src_s0, src_s1, src_s2: IN std_logic;
        des_A0, des_A1, des_A2: IN std_logic;
        CLK: IN std_logic;
        data_src: IN std_logic;
        data: IN std_logic_vector(15 downto 0);
        reg0, reg1, reg2, reg3, reg4, reg5, reg6, reg7: out STD_LOGIC_VECTOR (15
            downto 0));
    END COMPONENT;

    --Inputs
    signal src_s0: std_logic:= '0';
    signal src_s1: std_logic:= '0';
    signal src_s2: std_logic:= '0';
    signal des_A0: std_logic:= '0';
    signal des_A1: std_logic:= '0';
    signal des_A2: std_logic:= '0';
    signal CLK: std_logic:= '0';
    signal data_src: std_logic:= '0';
    signal data: std_logic_vector(15 downto 0):= (others => '0');

    --Outputs
    signal reg0, reg1, reg2, reg3, reg4, reg5, reg6, reg7: STD_LOGIC_VECTOR (15 downto 0);

    -- Clock period definitions
    constant CLK_period: time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: register_file PORT MAP (
        src_s0 => src_s0,
        src_s1 => src_s1,
        src_s2 => src_s2,
        des_A0 => des_A0,
        des_A1 => des_A1,
        des_A2 => des_A2,
        CLK => CLK,
        data_src => data_src,
        data => data,
        reg0 => reg0,
```

```

        reg1 => reg1,
        reg2 => reg2,
        reg3 => reg3,
        reg4 => reg4,
        reg5 => reg5,
        reg6 => reg6,
        reg7 => reg7);

-- Clock process definitions
CLK_process :process
begin
    CLK <= '0';
    wait for CLK_period/2;
    CLK <= '1';
    wait for CLK_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 10 ns;

    -- Q2(a) Loading straight into the registers
    src_S0<='0'; src_S1<='0'; src_S2<='0';
    data_src <= '0';
    data <= "0000000000000000";

    -- 0
    wait for CLK_period*3;
    des_A0<='0'; des_A1<='0'; des_A2<='0';

    -- 1
    wait for CLK_period*3;
    des_A0<='1'; des_A1<='0'; des_A2<='0';

    -- 2
    wait for CLK_period*3;
    des_A0<='0'; des_A1<='1'; des_A2<='0';

    -- 3
    wait for CLK_period*3;
    des_A0<='1'; des_A1<='1'; des_A2<='0';

    -- 4
    wait for CLK_period*3;
    des_A0<='0'; des_A1<='0'; des_A2<='1';

    -- 5
    wait for CLK_period*3;
    des_A0<='1'; des_A1<='0'; des_A2<='1';

    -- 6

```

```

wait for CLK_period*3;
des_A0<='0'; des_A1<='1'; des_A2<='1';

-- 7
wait for CLK_period*3;
des_A0<='1'; des_A1<='1'; des_A2<='1';

-- Q2(b) Loading from one register into the others
wait for CLK_period*3;

-- setup to read value from 0
des_A0<='0'; des_A1<='0'; des_A2<='0';
data <= "1111111111111111";
wait for CLK_period*3;
data_src <= '1';

-- 1
wait for CLK_period*3;
des_A0<='1'; des_A1<='0'; des_A2<='0';

-- 2
wait for CLK_period*3;
des_A0<='0'; des_A1<='1'; des_A2<='0';

-- 3
wait for CLK_period*3;
des_A0<='1'; des_A1<='1'; des_A2<='0';

-- 4
wait for CLK_period*3;
des_A0<='0'; des_A1<='0'; des_A2<='1';

-- 5
wait for CLK_period*3;
des_A0<='1'; des_A1<='0'; des_A2<='1';


-- 6
wait for CLK_period*3;
des_A0<='0'; des_A1<='1'; des_A2<='1';

-- 7
wait for CLK_period*3;
des_A0<='1'; des_A1<='1'; des_A2<='1';

wait;
end process;
END;
```
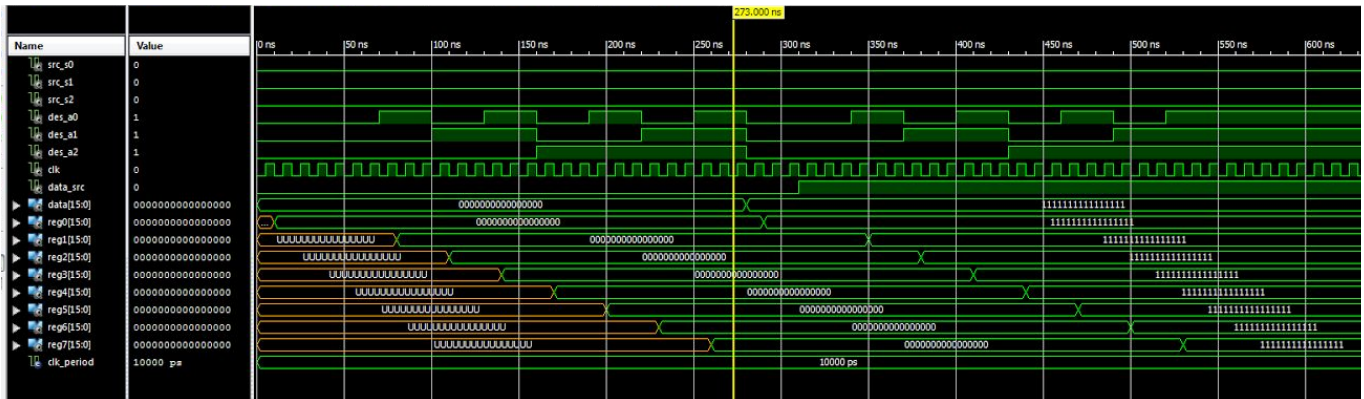
## 2.2 Register\_file Test Results

Loading raw data “0000000000000000” into the registers:



Loading saved data “1111111111111111” from reg0 into the other registers:

