

# Computer Architecture

## Project 1, Datapath Design, Part B

Joanna Whittam (15319524)

March 22<sup>nd</sup> 2017

## 1 Register file

### 1.1 Reg

#### 1.1.1 Reg Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity reg is
    Port ( D: in STD_LOGIC_VECTOR (15 downto 0);
          load, CLK: in STD_LOGIC;
          Q: out STD_LOGIC_VECTOR (15 downto 0) );
end reg;

architecture Behavioral of reg is

begin
    process(CLK)
    begin
        if (rising_edge(CLK)) then
            if load='1' then
                Q <= D after 5 ns;
            end if;
        end if;
    end process;
end Behavioral;
```

#### 1.1.2 Reg Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY reg_tb IS
END reg_tb;

ARCHITECTURE behavior OF reg_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT reg
    PORT( D: IN std_logic_vector(15 downto 0);
          load, CLK: IN std_logic;
          Q: OUT std_logic_vector(15 downto 0) );
    END COMPONENT;

    --Inputs
    signal D: std_logic_vector(15 downto 0) := (others => '0');
    signal load: std_logic := '0';
    signal CLK: std_logic := '0';

    --Outputs
    signal Q: std_logic_vector(15 downto 0);
```

```

-- Clock period definitions
constant CLK_period: time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)
ut: reg PORT MAP (
    D => D,
    load => load,
    CLK => CLK,
    Q => Q
);

-- Clock process definitions
CLK_process :process
begin
    CLK <= '0';
    wait for CLK_period/2;
    CLK <= '1';
    wait for CLK_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 50 ns.
    wait for 5 ns;

    D <= "0000000000001111";
    wait for CLK_period*20;
    load <= '1';
    wait for CLK_period*20;
    load <= '0';

    D <= "0000000011110000";
    wait for CLK_period*20;
    load <= '1';
    wait for CLK_period*20;
    load <= '0';

    D <= "0000111100000000";
    wait for CLK_period*20;
    load <= '1';
    wait for CLK_period*20;
    load <= '0';


    D <= "1111000000000000";
    wait for CLK_period*20;
    load <= '1';
    wait for CLK_period*20;
    load <= '0';
    wait;

end process;

END;

```

### 1.1.3 Reg Test Results

 

## 1.2 Decoder

### 1.2.1 Decoder Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity decoder_3to8 is
    Port ( A0,A1,A2: in  STD_LOGIC;
           Q0,Q1,Q2,Q3,Q4,Q5,Q6,Q7: out STD_LOGIC );
end decoder_3to8;

architecture Behavioral of decoder_3to8 is

begin
    Q0 <= ((not A2)      and (not A1)      and (not A0)) after 1 ns;
    Q1 <= ((not A2)      and (not A1)      and  A0) after 1 ns;
    Q2 <= ((not A2)      and  A1          and (not A0)) after 1 ns;
    Q3 <= ((not A2)      and  A1          and  A0) after 1 ns;
    Q4 <= (  A2          and (not A1)      and (not A0)) after 1 ns;
    Q5 <= (  A2          and (not A1)      and  A0) after 1 ns;
    Q6 <= (  A2          and  A1          and (not A0)) after 1 ns;
    Q7 <= (  A2          and  A1          and  A0) after 1 ns;
end Behavioral;
```

### 1.2.2 Decoder Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY decoder_3to8_tb IS
END decoder_3to8_tb;

ARCHITECTURE behavior OF decoder_3to8_tb IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT decoder_3to8
        PORT(
            A0,A1,A2: in  STD_LOGIC;
            Q0,Q1,Q2,Q3,Q4,Q5,Q6,Q7: out STD_LOGIC );
    END COMPONENT;

    --Inputs
    signal A0 : std_logic := '0';
    signal A1 : std_logic := '0';
    signal A2 : std_logic := '0';

    --Outputs
    signal Q0,Q1,Q2,Q3,Q4,Q5,Q6,Q7: std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: decoder_3to8 PORT MAP (
        A0 => A0,
        A1 => A1,
        A2 => A2,
        Q0 => Q0,
        Q1 => Q1,
        Q2 => Q2,
        Q3 => Q3,
        Q4 => Q4,
        Q5 => Q5,
        Q6 => Q6,
        Q7 => Q7
    );
```

```

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 10 ns.
    wait for 10 ns;

    -- 0
    A0<='0'; A1<='0'; A2<='0';
    wait for 100 ns;

    -- 1
    A0<='1'; A1<='0'; A2<='0';
    wait for 100 ns;

    -- 2
    A0<='0'; A1<='1'; A2<='0';
    wait for 100 ns;

    -- 3
    A0<='1'; A1<='1'; A2<='0';
    wait for 100 ns;

    -- 4
    A0<='0'; A1<='0'; A2<='1';
    wait for 100 ns;


    -- 5
    A0<='1'; A1<='0'; A2<='1';
    wait for 100 ns;

    -- 6
    A0<='0'; A1<='1'; A2<='1';
    wait for 100 ns;

    -- 7
    A0<='1'; A1<='1'; A2<='1';
    wait;
end process;
END;

```

### 1.2.3 Decoder Test Results

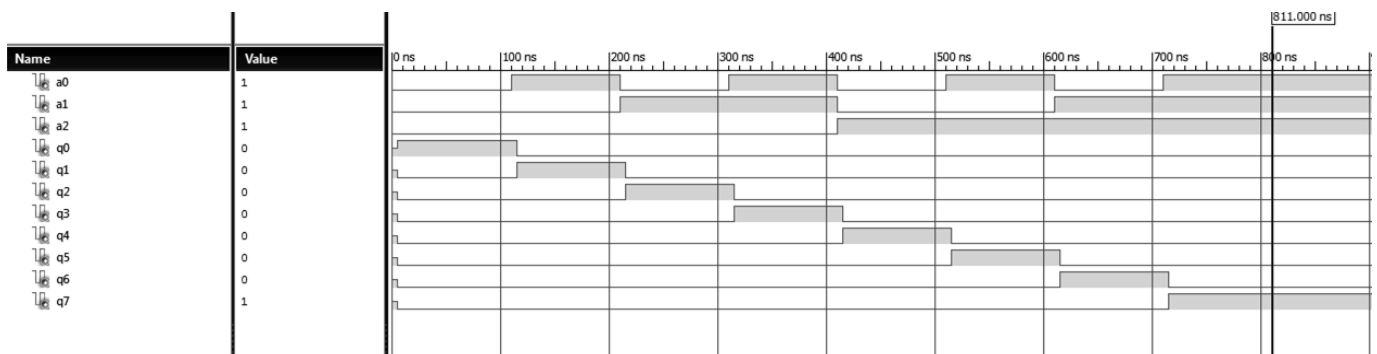

## 1.3 Mux8\_16bit

### 1.3.1 Mux8\_16bit Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux8_16bit is
    Port ( S0,S1,S2: in STD_LOGIC;
           In0,In1,In2,In3,In4,In5,In6,In7: in STD_LOGIC_VECTOR (15 downto 0);
           Z: out STD_LOGIC_VECTOR (15 downto 0));
end mux8_16bit;

architecture Behavioral of mux8_16bit is
begin
    Z <=      In0 after 5 ns when S2='0' and S1='0' and S0='0' else
              In1 after 5 ns when S2='0' and S1='0' and S0='1' else
              In2 after 5 ns when S2='0' and S1='1' and S0='0' else
              In3 after 5 ns when S2='0' and S1='1' and S0='1' else
              In4 after 5 ns when S2='1' and S1='0' and S0='0' else
              In5 after 5 ns when S2='1' and S1='0' and S0='1' else
              In6 after 5 ns when S2='1' and S1='1' and S0='0' else
              In7 after 5 ns when S2='1' and S1='1' and S0='1';
end Behavioral;
```

### 1.3.2 Mux8\_16bit Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mux8_16bit_tb IS
END mux8_16bit_tb;

ARCHITECTURE behavior OF mux8_16bit_tb IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT mux8_16bit
    PORT( S0,S1,S2: in  STD_LOGIC;
          In0,In1,In2,In3,In4,In5,In6,In7: in  STD_LOGIC_VECTOR (15 downto 0);
          Z: out STD_LOGIC_VECTOR (15 downto 0));
    END COMPONENT;

    --Inputs
    signal S0 : std_logic := '0';
    signal S1 : std_logic := '0';
    signal S2 : std_logic := '0';
    signal In0 : std_logic_vector(15 downto 0) := (others => '0');
    signal In1 : std_logic_vector(15 downto 0) := (others => '0');
    signal In2 : std_logic_vector(15 downto 0) := (others => '0');
    signal In3 : std_logic_vector(15 downto 0) := (others => '0');
    signal In4 : std_logic_vector(15 downto 0) := (others => '0');
    signal In5 : std_logic_vector(15 downto 0) := (others => '0');
    signal In6 : std_logic_vector(15 downto 0) := (others => '0');
    signal In7 : std_logic_vector(15 downto 0) := (others => '0');
    signal Z : std_logic_vector(15 downto 0) := (others => '0');

    BEGIN
        -- Instantiate the Unit Under Test (UUT)
        uut: mux8_16bit PORT MAP (
            S0 => S0,
            S1 => S1,
            S2 => S2,
            In0 => In0,
            In1 => In1,
```

```

        In2 => In2,
        In3 => In3,
        In4 => In4,
        In5 => In5,
        In6 => In6,
        In7 => In7,
        Z => Z
    );

    -- Stimulus process
    stim_proc: process
    begin
        In0 <= "00000000000000011";
        In1 <= "00000000000001100";
        In2 <= "00000000000110000";
        In3 <= "00000000011000000";
        In4 <= "00000001100000000";
        In5 <= "00001100000000000";
        In6 <= "00110000000000000";
        In7 <= "11000000000000000";
        wait for 100 ns;

        -- 0
        S0<='0'; S1<='0'; S2<='0';
        wait for 100 ns;

        -- 1
        S0<='1'; S1<='0'; S2<='0';
        wait for 100 ns;

        -- 2
        S0<= '0'; S1<='1'; S2<='0';
        wait for 100 ns;


        -- 3
        S0<= '1'; S1<='1'; S2<='0';
        wait for 100 ns;
        -- 4
        S0<= '0'; S1<='0'; S2<='1';
        wait for 100 ns;

        -- 5
        S0<= '1'; S1<='0'; S2<='1';
        wait for 100 ns;

        -- 6
        S0<= '0'; S1<='1'; S2<='1';
        wait for 100 ns;

        -- 7
        S0<='1'; S1<='1'; S2<='1';
        wait;
    end process;
END;
```

### 1.3.3 Mux8\_16bit Test Results

 

## 1.4 Register File

### 1.4.1 Register\_file Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity register_file_v2 is
    PORT( load_enable, CLK : in  STD_LOGIC;
          dest_select, Asel, Bsel : in  STD_LOGIC_VECTOR(2 downto 0);
          DData : in  STD_LOGIC_VECTOR (15 downto 0);
          AData, BData : out  STD_LOGIC_VECTOR (15 downto 0));
end register_file_v2;

architecture Behavioral of register_file_v2 is
--COMPONENTS
    component decoder_3to8 is
        Port ( A0,A1,A2: in  STD_LOGIC;
              Q0,Q1,Q2,Q3,Q4,Q5,Q6,Q7: out  STD_LOGIC );
    end component;

    component reg
        Port ( D: in  STD_LOGIC_VECTOR (15 downto 0);
              load, CLK: in  STD_LOGIC;
              Q: out  STD_LOGIC_VECTOR (15 downto 0) );
    end component;

    component mux8_16bit is
        Port ( S0,S1,S2: in  STD_LOGIC;
              In0,In1,In2,In3,In4,In5,In6,In7: in  STD_LOGIC_VECTOR (15 downto 0);
              Z: out  STD_LOGIC_VECTOR (15 downto 0));
    end component;

--SIGNALS
    signal load_r0,load_r1,load_r2,load_r3,load_r4,load_r5,load_r6,load_r7: std_logic;
    signal decode0_q, decode1_q, decode2_q, decode3_q, decode4_q, decode5_q, decode6_q,
          decode7_q: std_logic;
    signal reg0_q,reg1_q,reg2_q,reg3_q,reg4_q,reg5_q,reg6_q,reg7_q: std_logic_vector(15 downto 0);

begin
    --Decoder
    decoder: decoder_3to8 PORT MAP(
        A0 => dest_select(0),
        A1 => dest_select(1),
        A2 => dest_select(2),
        Q0 => decode0_q,
        Q1 => decode1_q,
        Q2 => decode2_q,

```

```

        Q3 => decode3_q,
        Q4 => decode4_q,
        Q5 => decode5_q,
        Q6 => decode6_q,
        Q7 => decode7_q
    );

load_r0 <= load_enable and decode0_q;
load_r1 <= load_enable and decode1_q;
load_r2 <= load_enable and decode2_q;
load_r3 <= load_enable and decode3_q;
load_r4 <= load_enable and decode4_q;
load_r5 <= load_enable and decode5_q;
load_r6 <= load_enable and decode6_q;
load_r7 <= load_enable and decode7_q;

reg00: reg PORT MAP(
    D => DData,
    load => load_r0,
    Clk => Clk,
    Q => reg0_q
);

reg01: reg PORT MAP(
    D => DData,
    load => load_r1,
    Clk => Clk,
    Q => reg1_q
);

reg02: reg PORT MAP(
    D => DData,
    load => load_r2,
    Clk => Clk,
    Q => reg2_q
);

reg03: reg PORT MAP(
    D => DData,
    load => load_r3,
    Clk => Clk,
    Q => reg3_q
);

reg04: reg PORT MAP(
    D => DData,
    load => load_r4,
    Clk => Clk,
    Q => reg4_q
);

reg05: reg PORT MAP(
    D => DData,
    load => load_r5,
    Clk => Clk,
    Q => reg5_q
);

reg06: reg PORT MAP(
    D => DData,
    load => load_r6,
    Clk => Clk,
    Q => reg6_q
);

reg07: reg PORT MAP(

```



```

        D => DData,
        load => load_r7,
        Clk => Clk,
        Q => reg7_q
    );

    A_mux8_16bit: mux8_16bit PORT MAP(
        S0 => Asel(0),
        S1 => Asel(1),
        S2 => Asel(2),
        In0 => reg0_q,
        In1 => reg1_q,
        In2 => reg2_q,
        In3 => reg3_q,
        In4 => reg4_q,
        In5 => reg5_q,
        In6 => reg6_q,
        In7 => reg7_q,
        Z => AData
    );

    B_mux8_16bit: mux8_16bit PORT MAP(
        S0 => Bsel(0),
        S1 => Bsel(1),
        S2 => Bsel(2),
        In0 => reg0_q,
        In1 => reg1_q,
        In2 => reg2_q,
        In3 => reg3_q,
        In4 => reg4_q,
        In5 => reg5_q,
        In6 => reg6_q,
        In7 => reg7_q,
        Z => BData
    );

end Behavioral;

```

### 1.4.2 Register\_file Test Bench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY register_file_v2_tb IS
END register_file_v2_tb;

ARCHITECTURE behavior OF register_file_v2_tb IS

    COMPONENT register_file_v2
    PORT( load_enable, CLK : in  STD_LOGIC;
          dest_select, Asel, Bsel : in  STD_LOGIC_VECTOR(2 downto 0);
          DData : in  STD_LOGIC_VECTOR (15 downto 0);
          AData, BData : out  STD_LOGIC_VECTOR (15 downto 0));
    END COMPONENT;

    --Inputs
    signal load_enable: std_logic := '0';
    signal CLK: std_logic:= '0';
    signal dest_select: std_logic_vector(2 downto 0) := (others => '0');
    signal Asel, Bsel: std_logic_vector(2 downto 0) := (others => '0');
    signal DData: std_logic_vector(15 downto 0) := (others => '0');
    --Outputs
    signal AData, BData : std_logic_vector(15 downto 0);

```

```

        -- Clock period definitions
        constant CLK_period: time := 10 ns;

BEGIN
    uut: register_file_v2 PORT MAP (
        load_enable => load_enable,
                        CLK => CLK,
        dest_select => dest_select,
        Asel => Asel,
        Bsel => Bsel,
        DData => DData,
        AData => AData,
        BData => BData
    );

    CLK_process :process
    begin
        CLK <= '0';
        wait for CLK_period/2;
        CLK <= '1';
        wait for CLK_period/2;
    end process;

    stim_proc: process
    begin

        wait for 10 ns;
        load_enable <= '1';
        DData <= "0000000000000011";
        dest_select <= "000";

        --set registers to unique values
        for i in 0 to 7 loop
            wait for CLK_period*2;
            dest_select <= STD_LOGIC_VECTOR (unsigned(dest_select) + 1);
            wait for CLK_period*2;
            DData <= STD_LOGIC_VECTOR (unsigned(DData) +16);
            wait for CLK_period*2;
        end loop;


        --read each register from A and B outputs
        Asel <= "000";
        Bsel <= "000";
        for i in 0 to 7 loop
            wait for CLK_period*3;
            Asel <= STD_LOGIC_VECTOR (unsigned(Asel) + 1);
            wait for CLK_period;
            Bsel <= STD_LOGIC_VECTOR (unsigned(Bsel) + 1);
        end loop;

        wait;
    end process;

END;

```

### 1.4.2 Register\_file Test Results

 

## 2 Function Unit

## 2.1 Zero Detect

### 2.1.1 Zero\_detect code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity zero_detect_16 is
    Port (    data : in  STD_LOGIC_VECTOR (15 downto 0);
            z : out STD_LOGIC);
end zero_detect_16;

architecture Behavioral of zero_detect_16 is

begin
    z    <=  '1' after 1 ns when data="0000000000000000"
            else '0';
end Behavioral;
```

### 2.1.2 Zero\_detect Test Bench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY zero_detect_tb IS
END zero_detect_tb;

ARCHITECTURE behavior OF zero_detect_tb IS

-- Component Declaration for the Unit Under Test (UUT)
COMPONENT zero_detect_16
    PORT(
        data : IN  std_logic_vector(15 downto 0);
        z : OUT  std_logic
    );
END COMPONENT;

--Inputs
    signal data : std_logic_vector(15 downto 0) := (others => '0');

--Outputs
    signal z : std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: zero_detect_16 PORT MAP (

```

```

        data => data,
        z => z
    );

-- Stimulus process
stim_proc: process
begin
wait for 100 ns;
    data <= "0000000000000001";
    wait for 10 ns;

    data <= "0000000000000000";
    wait for 10 ns;

    data <= "1000000000000000";
    wait for 10 ns;


    data <= "0000000000000000";
    wait for 10 ns;

    data <= "1111111111111111";
    wait for 10 ns;

    data <= "0000000000000000";
    wait for 10 ns;
    Wait;
end process;
END;

```

## 2.1.3 Zero\_detect Test Results

 

## 2.2 Mux2\_16bit

In my file this entity is incorrectly named as mux2\_4bit. This will be changed in later versions of the code.

### 2.2.1 Mux2\_16bit Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux2_16bit is
    Port ( S: in  STD_LOGIC;
          In0, In1: in  STD_LOGIC_VECTOR (15 downto 0);
          Z: out  STD_LOGIC_VECTOR (15 downto 0));
end mux2_16bit;

architecture Behavioral of mux2_16bit is

begin
    Z <= In0 after 1 ns when S='0' else
          In1 after 1 ns when S='1';
end Behavioral;

```

## 2.2.2 Mux2\_16bit Test Bench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mux2_4bit_tb IS
END mux2_4bit_tb;

ARCHITECTURE behavior OF mux2_4bit_tb IS
    COMPONENT mux2_4bit
    PORT(
        S: in STD_LOGIC;
        In0, In1: in STD_LOGIC_VECTOR (15 downto 0);
        Z: out STD_LOGIC_VECTOR (15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal S : std_logic := '0';
    signal In0 : std_logic_vector(15 downto 0) := (others => '0');
    signal In1 : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal Z : std_logic_vector(15 downto 0);

BEGIN


    -- Instantiate the Unit Under Test (UUT)
    uut: mux2_bit PORT MAP (
        S => S,
        In0 => In0,
        In1 => In1,
        Z => Z
    );

    -- Stimulus process
    stim_proc: process
    begin
        In0 <= "0000000000000000";
        In1 <= "1111111111111111";

        S <= '0';
        wait for 100 ns;

        S <= '1';
        wait for 100 ns;
    end process;
END;
```

## 2.2.3 Mux2\_16bit Test Results

 

## 2.3 Mux16\_1bit

### 2.3.1 Mux16\_1bit Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity mux16_1bit is
    Port ( in0,in1,in2,in3,in4,in5,in6,in7,in8,in9,in10,in11,in12,in13,in14,in15: in STD_LOGIC;
```

```

        s0,s1,s2,s3: in STD_LOGIC;
        z: out STD_LOGIC);
end mux16_1bit;

```

architecture Behavioral of mux16\_1bit is

```

begin
Z <=   in0 after 5 ns    when s3='0'    and s2='0'    and s1='0'    and s0='0'    else
        in1 after 5 ns    when s3='0'    and s2='0'    and s1='0'    and s0='1'    else
        in2 after 5 ns    when s3='0'    and s2='0'    and s1='1'    and s0='0'    else
        in3 after 5 ns    when s3='0'    and s2='0'    and s1='1'    and s0='1'    else
        in4 after 5 ns    when s3='0'    and s2='1'    and s1='0'    and s0='0'    else
        in5 after 5 ns    when s3='0'    and s2='1'    and s1='0'    and s0='1'    else
        in6 after 5 ns    when s3='0'    and s2='1'    and s1='1'    and s0='0'    else
        in7 after 5 ns    when s3='0'    and s2='1'    and s1='1'    and s0='1'    else
        in8 after 5 ns    when s3='1'    and s2='0'    and s1='0'    and s0='0'    else
        in9 after 5 ns    when s3='1'    and s2='0'    and s1='0'    and s0='1'    else
        in10 after 5 ns   when s3='1'    and s2='0'    and s1='1'    and s0='0'    else
        in11 after 5 ns   when s3='1'    and s2='0'    and s1='1'    and s0='1'    else
        in12 after 5 ns   when s3='1'    and s2='1'    and s1='0'    and s0='0'    else
        in13 after 5 ns   when s3='1'    and s2='1'    and s1='0'    and s0='1'    else
        in14 after 5 ns   when s3='1'    and s2='1'    and s1='1'    and s0='0'    else
        in15 after 5 ns   when s3='1'    and s2='1'    and s1='1'    and s0='1';

```

end Behavioral;

### 2.3.2 Mux16\_1bit Test Bench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

ENTITY mux16_1bit_tb IS
END mux16_1bit_tb;

```

ARCHITECTURE behavior OF mux16\_1bit\_tb IS

```

COMPONENT mux16_1bit
    PORT(   in0,in1,in2,in3,in4,in5,in6,in7,in8,in9,in10,in11,in12,in13,in14,in15: in STD_LOGIC;
           s0,s1,s2,s3: in STD_LOGIC;
           z : out std_logic );
END COMPONENT;

```

--Inputs

```

signal in0,in1,in2,in3,in4,in5,in6,in7,in8,in9,in10,in11,in12,in13,in14,in15 : std_logic := '0';
signal s0,s1,s2,s3 : std_logic := '0';

```

--Outputs

```

signal z : std_logic;

```

BEGIN

```

uut: mux16_1bit PORT MAP (
    in0 => in0,
    in1 => in1,
    in2 => in2,
    in3 => in3,
    in4 => in4,
    in5 => in5,
    in6 => in6,
    in7 => in7,
    in8 => in8,
    in9 => in9,
    in10 => in10,
    in11 => in11,
    in12 => in12,
    in13 => in13,

```

```

in14 => in14,
in15 => in15,
s0 => s0,
s1 => s1,
s2 => s2,
s3 => s3,
z => z
);

stim_proc: process
begin
    wait for 100 ns;
    in0 <= '0';
    in1 <= '0';
    in2 <= '1';
    in3 <= '1';
    in4 <= '0';
    in5 <= '0';
    in6 <= '1';
    in7 <= '1';
    in8 <= '0';
    in9 <= '0';
    in10 <= '1';
    in11 <= '1';
    in12 <= '0';
    in13 <= '0';
    in14 <= '1';
    in15 <= '1';

    s0 <= '0';    s1 <= '0';    s2 <= '0';    s3 <= '0';    wait for 10 ns;
    s0 <= '1';    s1 <= '0';    s2 <= '0';    s3 <= '0';    wait for 10 ns;
    s0 <= '0';    s1 <= '1';    s2 <= '0';    s3 <= '0';    wait for 10 ns;
    s0 <= '1';    s1 <= '1';    s2 <= '0';    s3 <= '0';    wait for 10 ns;
    s0 <= '0';    s1 <= '0';    s2 <= '1';    s3 <= '0';    wait for 10 ns;
    s0 <= '1';    s1 <= '0';    s2 <= '1';    s3 <= '0';    wait for 10 ns;
    s0 <= '0';    s1 <= '1';    s2 <= '1';    s3 <= '0';    wait for 10 ns;
    s0 <= '1';    s1 <= '1';    s2 <= '1';    s3 <= '0';    wait for 10 ns;
    s0 <= '0';    s1 <= '0';    s2 <= '0';    s3 <= '1';    wait for 10 ns;
    s0 <= '1';    s1 <= '0';    s2 <= '0';    s3 <= '1';    wait for 10 ns;
    s0 <= '0';    s1 <= '1';    s2 <= '0';    s3 <= '1';    wait for 10 ns;
    s0 <= '1';    s1 <= '1';    s2 <= '0';    s3 <= '1';    wait for 10 ns;
    s0 <= '0';    s1 <= '0';    s2 <= '1';    s3 <= '1';    wait for 10 ns;
    s0 <= '1';    s1 <= '0';    s2 <= '1';    s3 <= '1';    wait for 10 ns;
    s0 <= '0';    s1 <= '1';    s2 <= '1';    s3 <= '1';    wait for 10 ns;
    s0 <= '1';    s1 <= '1';    s2 <= '1';    s3 <= '1';    wait for 10 ns;
    wait;
end process;

END;
```

### 2.3.3 Mux16\_1bit Test Results



## 2.4 Shifter\_16bit

### 2.4.1 Shifter\_16bit Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity shifter_16bit is
    Port ( input: in STD_LOGIC_VECTOR(15 downto 0);
          sel0,sel1,sel2,sel3 : in STD_LOGIC;
          y: out STD_LOGIC_VECTOR(15 downto 0) );
end shifter_16bit;

architecture Behavioral of shifter_16bit is
--COMPONENTS
    component mux16_1bit is
        Port ( in0,in1,in2,in3,in4,in5,in6,in7,in8,in9,in10,in11,in12,in13,in14,in15: in STD_LOGIC;
              s0,s1,s2,s3: in STD_LOGIC;
              z: out STD_LOGIC );
    end component;

begin
-- PORT MAPS
    mux0: mux16_1bit port map (
        in0 => input(0),
        in1 => input(15),
        in2 => input(14),
        in3 => input(13),
        in4 => input(12),
        in5 => input(11),
        in6 => input(10),
        in7 => input(9),
        in8 => input(8),
        in9 => input(7),
        in10 => input(6),
        in11 => input(5),
        in12 => input(4),
        in13 => input(3),
        in14 => input(2),
        in15 => input(1),
        s0 => sel0,
        s1 => sel1,
```



```

        s2 => sel2,
        s3 => sel3,
        z => y(0)
    );

mux1: mux16_1bit port map (
    in0 => input(1),
    in1 => input(0),
    in2 => input(15),
    in3 => input(14),
    in4 => input(13),
    in5 => input(12),
    in6 => input(11),
    in7 => input(10),
    in8 => input(9),
    in9 => input(8),
    in10 => input(7),
    in11 => input(6),
    in12 => input(5),
    in13 => input(4),
    in14 => input(3),
    in15 => input(2),
    s0 => sel0,
    s1 => sel1,
    s2 => sel2,
    s3 => sel3,
    z => y(1)
);

mux2: mux16_1bit port map (
    in0 => input(2),
    in1 => input(1),
    in2 => input(0),
    in3 => input(15),
    in4 => input(14),
    in5 => input(13),
    in6 => input(12),
    in7 => input(11),
    in8 => input(10),
    in9 => input(9),
    in10 => input(8),
    in11 => input(7),
    in12 => input(6),
    in13 => input(5),
    in14 => input(4),
    in15 => input(3),
    s0 => sel0,
    s1 => sel1,
    s2 => sel2,
    s3 => sel3,
    z => y(2)
);

mux3: mux16_1bit port map (
    in0 => input(3),
    in1 => input(2),
    in2 => input(1),
    in3 => input(0),
    in4 => input(15),
    in5 => input(14),
    in6 => input(13),
    in7 => input(12),
    in8 => input(11),
    in9 => input(10),
    in10 => input(9),
    in11 => input(8),

```

```

        in12 => input(7),
        in13 => input(6),
        in14 => input(5),
        in15 => input(4),
        s0 => sel0,
        s1 => sel1,
        s2 => sel2,
        s3 => sel3,
        z => y(3)
    );

mux4: mux16_1bit port map (
    in0 => input(4),
    in1 => input(3),
    in2 => input(2),
    in3 => input(1),
    in4 => input(0),
    in5 => input(15),
    in6 => input(14),
    in7 => input(13),
    in8 => input(12),
    in9 => input(11),
    in10 => input(10),
    in11 => input(9),
    in12 => input(8),
    in13 => input(7),
    in14 => input(6),
    in15 => input(5),
    s0 => sel0,
    s1 => sel1,
    s2 => sel2,
    s3 => sel3,
    z => y(4)
);

mux5: mux16_1bit port map (
    in0 => input(5),
    in1 => input(4),
    in2 => input(3),
    in3 => input(2),
    in4 => input(1),
    in5 => input(0),
    in6 => input(15),
    in7 => input(14),
    in8 => input(13),
    in9 => input(12),
    in10 => input(11),
    in11 => input(10),
    in12 => input(9),
    in13 => input(8),
    in14 => input(7),
    in15 => input(6),
    s0 => sel0,
    s1 => sel1,
    s2 => sel2,
    s3 => sel3,
    z => y(5)
);

mux6: mux16_1bit port map (
    in0 => input(6),
    in1 => input(5),
    in2 => input(4),
    in3 => input(3),
    in4 => input(2),
    in5 => input(1),

```

```

        in6 => input(0),
        in7 => input(15),
        in8 => input(14),
        in9 => input(13),
        in10 => input(12),
        in11 => input(11),
        in12 => input(10),
        in13 => input(9),
        in14 => input(8),
        in15 => input(7),
        s0 => sel0,
        s1 => sel1,
        s2 => sel2,
        s3 => sel3,
        z => y(6)
    );

```

```

mux7: mux16_1bit port map (
    in0 => input(7),
    in1 => input(6),
    in2 => input(5),
    in3 => input(4),
    in4 => input(3),
    in5 => input(2),
    in6 => input(1),
    in7 => input(0),
    in8 => input(15),
    in9 => input(14),
    in10 => input(13),
    in11 => input(12),
    in12 => input(11),
    in13 => input(10),
    in14 => input(9),
    in15 => input(8),
    s0 => sel0,
    s1 => sel1,
    s2 => sel2,
    s3 => sel3,
    z => y(7)
);

```

```

mux8: mux16_1bit port map (
    in0 => input(8),
    in1 => input(7),
    in2 => input(6),
    in3 => input(5),
    in4 => input(4),
    in5 => input(3),
    in6 => input(2),
    in7 => input(1),
    in8 => input(0),
    in9 => input(15),
    in10 => input(14),
    in11 => input(13),
    in12 => input(12),
    in13 => input(11),
    in14 => input(10),
    in15 => input(9),
    s0 => sel0,
    s1 => sel1,
    s2 => sel2,
    s3 => sel3,
    z => y(8)
);

```

```

mux9: mux16_1bit port map (

```

```

        in0 => input(9),
        in1 => input(8),
        in2 => input(7),
        in3 => input(6),
        in4 => input(5),
        in5 => input(4),
        in6 => input(3),
        in7 => input(2),
        in8 => input(1),
        in9 => input(0),
        in10=> input(15),
        in11 => input(14),
        in12 => input(13),
        in13 => input(12),
        in14 => input(11),
        in15 => input(10),
        s0 => sel0,
        s1 => sel1,
        s2 => sel2,
        s3 => sel3,
        z => y(9)
    );

```

```

mux10: mux16_1bit port map (
    in0 => input(10),
    in1 => input(9),
    in2 => input(8),
    in3 => input(7),
    in4 => input(6),
    in5 => input(5),
    in6 => input(4),
    in7 => input(3),
    in8 => input(2),
    in9 => input(1),
    in10 => input(0),
    in11 => input(15),
    in12 => input(14),
    in13 => input(13),
    in14 => input(12),
    in15 => input(11),
    s0 => sel0,
    s1 => sel1,
    s2 => sel2,
    s3 => sel3,
    z => y(10)
);

```

```

mux11: mux16_1bit port map (
    in0 => input(11),
    in1 => input(10),
    in2 => input(9),
    in3 => input(8),
    in4 => input(7),
    in5 => input(6),
    in6 => input(5),
    in7 => input(4),
    in8 => input(3),
    in9 => input(2),
    in10 => input(1),
    in11 => input(0),
    in12 => input(15),
    in13 => input(14),
    in14 => input(13),
    in15 => input(12),
    s0 => sel0,
    s1 => sel1,

```

```

        s2 => sel2,
        s3 => sel3,
        z => y(11)
    );

mux12: mux16_1bit port map (
    in0 => input(12),
    in1 => input(11),
    in2 => input(10),
    in3 => input(9),
    in4 => input(8),
    in5 => input(7),
    in6 => input(6),
    in7 => input(5),
    in8 => input(4),
    in9 => input(3),
    in10 => input(2),
    in11 => input(1),
    in12 => input(0),
    in13 => input(15),
    in14 => input(14),
    in15 => input(13),
    s0 => sel0,
    s1 => sel1,
    s2 => sel2,
    s3 => sel3,
    z => y(12)
);

mux13: mux16_1bit port map (
    in0 => input(13),
    in1 => input(12),
    in2 => input(11),
    in3 => input(10),
    in4 => input(9),
    in5 => input(8),
    in6 => input(7),
    in7 => input(6),
    in8 => input(5),
    in9 => input(4),
    in10 => input(3),
    in11 => input(2),
    in12 => input(1),
    in13 => input(0),
    in14 => input(15),
    in15 => input(14),
    s0 => sel0,
    s1 => sel1,
    s2 => sel2,
    s3 => sel3,
    z => y(13)
);

mux14: mux16_1bit port map (
    in0 => input(14),
    in1 => input(13),
    in2 => input(12),
    in3 => input(11),
    in4 => input(10),
    in5 => input(9),
    in6 => input(8),
    in7 => input(7),
    in8 => input(6),
    in9 => input(5),
    in10 => input(4),
    in11 => input(3),
    in12 => input(2),

```

```

        in13 => input(1),
        in14 => input(0),
        in15 => input(15),
        s0 => sel0,
        s1 => sel1,
        s2 => sel2,
        s3 => sel3,
        z => y(14)
    );

mux15: mux16_1bit port map (
    in0 => input(15),
    in1 => input(14),
    in2 => input(13),
    in3 => input(12),
    in4 => input(11),
    in5 => input(10),
    in6 => input(9),
    in7 => input(8),
    in8 => input(7),
    in9 => input(6),
    in10 => input(5),
    in11 => input(4),
    in12 => input(3),
    in13 => input(2),
    in14 => input(1),
    in15 => input(0),
    s0 => sel0,
    s1 => sel1,
    s2 => sel2,
    s3 => sel3,
    z => y(15)
);
end Behavioral;

```

## 2.4.2 Shifter\_16bit Test Bench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY testbench IS
END testbench;

ARCHITECTURE behavior OF testbench IS

    component shifter_16bit
    Port ( input: in STD_LOGIC_VECTOR(15 downto 0);
          sel0,sel1,sel2,sel3 : in STD_LOGIC;
          y: out STD_LOGIC_VECTOR(15 downto 0) );
    end component;

    -- SIGNALS
    signal input: std_logic_vector(15 downto 0) := (others => '0');
    signal sel0,sel1,sel2,sel3 : STD_LOGIC := '0';
    signal y: std_logic_vector(15 downto 0);

    BEGIN
        uut: shifter_16bit PORT MAP(
            input => input,
            sel0 => sel0,
            sel1 => sel1,
            sel2 => sel2,
            sel3 => sel3,
            y => y
        );
    END

```

```
tb : PROCESS  
BEGIN
```

```
    wait for 10 ns;  
    input <= "0000000000000001";  
    sel0 <= '0';  
    sel1 <= '0';  
    sel2 <= '0';  
    sel3 <= '0';
```

```
    wait for 10 ns;  
    sel0 <= '1';  
    sel1 <= '0';  
    sel2 <= '0';  
    sel3 <= '0';
```

```
    wait for 10 ns;  
    sel0 <= '0';  
    sel1 <= '1';  
    sel2 <= '0';  
    sel3 <= '0';
```

```
    wait for 10 ns;  
    sel0 <= '1';  
    sel1 <= '1';  
    sel2 <= '0';  
    sel3 <= '0';
```

```
    wait for 10 ns;  
    sel0 <= '0';  
    sel1 <= '0';  
    sel2 <= '1';  
    sel3 <= '0';
```

```
    wait for 10 ns;  
    sel0 <= '1';  
    sel1 <= '0';  
    sel2 <= '1';  
    sel3 <= '0';
```

```
    wait for 10 ns;  
    sel0 <= '0';  
    sel1 <= '1';  
    sel2 <= '1';  
    sel3 <= '0';
```

```
    wait for 10 ns;  
    sel0 <= '1';  
    sel1 <= '1';  
    sel2 <= '1';  
    sel3 <= '0';
```

```
    wait for 10 ns;  
    sel0 <= '0';  
    sel1 <= '0';  
    sel2 <= '0';  
    sel3 <= '1';
```

```
    wait for 10 ns;  
    sel0 <= '1';  
    sel1 <= '0';  
    sel2 <= '0';  
    sel3 <= '1';
```

```
    wait for 10 ns;
```

```

sel0 <= '0';
sel1 <= '1';
sel2 <= '0';
sel3 <= '1';

wait for 10 ns;
sel0 <= '1';
sel1 <= '1';
sel2 <= '0';
sel3 <= '1';

wait for 10 ns;
sel0 <= '0';
sel1 <= '0';
sel2 <= '1';
sel3 <= '1';

wait for 10 ns;
sel0 <= '1';
sel1 <= '0';
sel2 <= '1';
sel3 <= '1';

wait for 10 ns;
sel0 <= '0';
sel1 <= '1';
sel2 <= '1';
sel3 <= '1';

wait for 10 ns;
sel0 <= '1';
sel1 <= '1';
sel2 <= '1';
sel3 <= '1';

wait;


```

```

END PROCESS tb;
END;

```

## 2.4.3 Shifter\_16bit Test Results

 

## 2.5 Full\_adder

### 2.5.1 Full\_adder Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity full_adder is
    Port ( A: in  STD_LOGIC;
          B: in  STD_LOGIC;
          c_in: in  STD_LOGIC;
          c_out: out STD_LOGIC;
          Sum: out STD_LOGIC);
end full_adder;

```



architecture Behavioral of full\_adder is

```
begin
c_out   <= (A and B) or ((A xor B) and c_in)after 1 ns;
Sum     <= ((A xor B) xor c_in)                after 1 ns;

end Behavioral;
```

## 2.5.2 Full\_adder Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
ENTITY full_adder_tb IS
END full_adder_tb;
```

```
ARCHITECTURE behavior OF full_adder_tb IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT full_adder
PORT(
  A : IN  std_logic;
  B : IN  std_logic;
  c_in : IN  std_logic;
  c_out : OUT std_logic;
  Sum : OUT std_logic
);
END COMPONENT;
```

```
--Inputs
```

```
signal A : std_logic := '0';
signal B : std_logic := '0';
signal c_in : std_logic := '0';
```

```
--Outputs
```

```
signal c_out : std_logic;
signal Sum : std_logic;
```

```
BEGIN
```

```
  uut: full_adder PORT MAP (
    A => A,
    B => B,
    c_in => c_in,
    c_out => c_out,
    Sum => Sum
  );
```

```
  stim_proc: process
```

```
  begin
```

```
    wait for 100 ns;
    A <= '0';
    B <= '0';
    c_in <= '1';
```

```
    --loop through A values
```

```
    for i in 0 to 1 loop
```

```
      --loop through B values
```

```
      for j in 0 to 1 loop
```

```


--loop through c_in values
for k in 0 to 1 loop
    wait for 10 ns;
    c_in <= not c_in;
end loop;
B <= not B;
end loop;
A <= not A;
end loop;

wait;
end process;

END;

```

## 2.5.3 Full\_adder Test Results

 

## 2.6 Ripple\_adder\_16bit

### 2.6.1 Ripple\_adder\_16bit Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ripple_adder_16bit is
    Port ( Ain, Bin : in  STD_LOGIC_VECTOR (15 downto 0);
          C_in : in  STD_LOGIC; -- TODO: should this be A_in?
          C_out : out STD_LOGIC;
          Z : out STD_LOGIC_VECTOR (15 downto 0));
end ripple_adder_16bit;

architecture Behavioral of ripple_adder_16bit is
    -- COMPONENTS
    component full_adder is
        Port ( A: in  STD_LOGIC;
              B: in  STD_LOGIC;
              c_in: in  STD_LOGIC;
              c_out: out STD_LOGIC;
              Sum: out STD_LOGIC);
    end component;

    -- SIGNALS
    signal c1, c2, c3, c4, c5, c6, c7, c8, c9, c10, c11, c12, c13, c14, c15: STD_LOGIC;

```

```

begin
-- PORT MAPS
    full0: full_adder port map (
        A => Ain(0),
        B => Bin(0),
        c_in => C_in,
        c_out => c1,
        Sum => Z(0)
    );

    full1: full_adder port map (
        A => Ain(1),
        B => Bin(1),
        c_in => c1,
        c_out => c2,
        Sum => Z(1)
    );

    full2: full_adder port map (
        A => Ain(2),
        B => Bin(2),
        c_in => c2,
        c_out => c3,
        Sum => Z(2)
    );

    full3: full_adder port map (
        A => Ain(3),
        B => Bin(3),
        c_in => c3,
        c_out => c4,
        Sum => Z(3)
    );

    full4: full_adder port map (
        A => Ain(4),
        B => Bin(4),
        c_in => c4,
        c_out => c5,
        Sum => Z(4)
    );

    full5: full_adder port map (
        A => Ain(5),
        B => Bin(5),
        c_in => c5,
        c_out => c6,
        Sum => Z(5)
    );

    full6: full_adder port map (
        A => Ain(6),
        B => Bin(6),
        c_in => c6,
        c_out => c7,
        Sum => Z(6)
    );

```

```
full7: full_adder port map (  
    A => Ain(7),  
    B => Bin(7),  
    c_in => c7,  
    c_out => c8,  
    Sum => Z(7)  
);
```

```
full8: full_adder port map (  
    A => Ain(8),  
    B => Bin(8),  
    c_in => c8,  
    c_out => c9,  
    Sum => Z(8)  
);
```

```
full9: full_adder port map (  
    A => Ain(9),  
    B => Bin(9),  
    c_in => c9,  
    c_out => c10,  
    Sum => Z(9)  
);
```

```
full10: full_adder port map (  
    A => Ain(10),  
    B => Bin(10),  
    c_in => c10,  
    c_out => c11,  
    Sum => Z(10)  
);
```

```
full11: full_adder port map (  
    A => Ain(11),  
    B => Bin(11),  
    c_in => c11,  
    c_out => c12,  
    Sum => Z(11)  
);
```

```
full12: full_adder port map (  
    A => Ain(12),  
    B => Bin(12),  
    c_in => c12,  
    c_out => c13,  
    Sum => Z(12)  
);
```

```
full13: full_adder port map (  
    A => Ain(13),  
    B => Bin(13),  
    c_in => c13,  
    c_out => c14,  
    Sum => Z(13)  
);
```

```

full14: full_adder port map (
    A => Ain(14),
    B => Bin(14),
    c_in => c14,
    c_out => c15,
    Sum => Z(14)
);

full15: full_adder port map (
    A => Ain(15),
    B => Bin(15),
    c_in => c15,
    c_out => C_out,
    Sum => Z(15)
);

end Behavioral;

```

## 2.6.2 Ripple\_adder\_16bit Test Bench

## 2.6.3 Ripple\_adder\_16bit Test Results

# 2.7 Arithmetic\_logic\_unit

## 2.7.1 Arithmetic\_logic\_unit Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity arithmetic_logic_unit is
    Port ( dataA, dataB : in  STD_LOGIC_VECTOR (15 downto 0);
          FS_code : in  STD_LOGIC_VECTOR (4 downto 0);
          V, C_out : out  STD_LOGIC;
          dataG : out  STD_LOGIC_VECTOR (15 downto 0));
end arithmetic_logic_unit;

architecture Behavioral of arithmetic_logic_unit is

begin
    --assign dataG
    dataG <= dataA
        after 5 ns when FS_code="00000" else
        std_logic_vector( unsigned(dataA) + 1)
        after 5 ns when FS_code="00001" else
        std_logic_vector( unsigned(dataA) + unsigned(dataB))
        after 5 ns when FS_code="00010" else
        std_logic_vector( unsigned(dataA) + unsigned(dataB) + 1)
        after 5 ns when FS_code="00011" else
        std_logic_vector( unsigned(dataA) + unsigned(not dataB))
        after 5 ns when FS_code="00100" else
        std_logic_vector( unsigned(dataA) + unsigned(not dataB) + 1)
        after 5 ns when FS_code="00101"
        else
        std_logic_vector( unsigned(dataA) - 1)
        after 5 ns when FS_code="00110" else
        dataA
        after 5 ns when FS_code="00111" else
        dataA and dataB
        after 5 ns when FS_code="01000" else
        dataA or dataB
        after 5 ns when FS_code="01010" else
        dataA xor dataB
        after 5 ns when FS_code="01100" else
        not dataA
        after 5 ns when FS_code="01110";

```

```
--assign flags
V <= '0';
C_out <= '0';
```

```
end Behavioral;
```

## 2.7.2 Arithmetic\_logic\_unit Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY ALU_tb IS
END ALU_tb;
```

```
ARCHITECTURE behavior OF ALU_tb IS
```

```
    COMPONENT arithmetic_logic_unit
    PORT(
        dataA, dataB : IN  std_logic_vector(15 downto 0);
        FS_code : IN  std_logic_vector(4 downto 0);
        V, C_out : OUT std_logic;
        dataG : OUT  std_logic_vector(15 downto 0) );
    END COMPONENT;
```

```
--Inputs
```

```
signal dataA : std_logic_vector(15 downto 0) := (others => '0');
signal dataB : std_logic_vector(15 downto 0) := (others => '0');
signal FS_code : std_logic_vector(4 downto 0) := (others => '0');
```

```
--Outputs
```

```
signal V : std_logic;
signal C_out : std_logic;
signal dataG : std_logic_vector(15 downto 0);
```

```
BEGIN
```

```
    uut: arithmetic_logic_unit PORT MAP (
        dataA => dataA,
        dataB => dataB,
        FS_code => FS_code,
        V => V,
        C_out => C_out,
        dataG => dataG
    );
```

```
    stim_proc: process
```

```
    begin
```

```
        wait for 10 ns;
        dataA <= "0000111100000000";
        dataB <= "0000000011110000";
```

```
        wait for 10 ns;    FS_code <= "00000";
        wait for 10 ns;    FS_code <= "00001";
        wait for 10 ns;    FS_code <= "00010";
        wait for 10 ns;    FS_code <= "00011";
        wait for 10 ns;    FS_code <= "00100";
        wait for 10 ns;    FS_code <= "00101";
        wait for 10 ns;    FS_code <= "00110";
        wait for 10 ns;    FS_code <= "00111";
```

```

        wait for 10 ns;    FS_code <= "01000";
        wait for 10 ns;    FS_code <= "01010";
        wait for 10 ns;    FS_code <= "01100";
        wait for 10 ns;    FS_code <= "01110";
        wait;
    end process;


```

```

END;

```
 
## 2.7.3 Arithmetic\_logic\_unit Test Results



## 2.8 Function\_unit

### 2.8.1 Function\_unit Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

entity function\_unit is

```

Port ( busA, busB : in  STD_LOGIC_VECTOR (15 downto 0);
      Fsel : in  STD_LOGIC_VECTOR (4 downto 0);
      V, C, N, Z : out  STD_LOGIC;
      F : out  STD_LOGIC_VECTOR (15 downto 0));
end function_unit;

```

architecture Behavioral of function\_unit is

-- COMPONENTS

```

    component shifter_16bit is
    Port(   input: in STD_LOGIC(15 to 0);
          sel0,sel1,sel2,sel3 : in  STD_LOGIC;
          y: out STD_LOGIC(15 to 0));
    end component;

```

```

    component zero_detect_16 is
    Port (   data : in  STD_LOGIC_VECTOR (15 downto 0);
          z : out  STD_LOGIC);
    end component;

```

```

    component mux2_16bit is
    Port (   S: in  STD_LOGIC;
          In0, In1: in  STD_LOGIC_VECTOR (15 downto 0);
          Z: out  STD_LOGIC_VECTOR (15 downto 0));
    end component;

```

```

    component arithmetic_logic_unit is
    Port (   busA, busB : in  STD_LOGIC_VECTOR (15 downto 0);
          G_sel : in  STD_LOGIC_VECTOR (4 downto 0);
          V, C : out  STD_LOGIC;
          G : out  STD_LOGIC_VECTOR (15 downto 0));

```

```

        end component;

        -- SIGNALS
        signal ALU_out, shifter_out: STD_LOGIC_VECTOR (15 downto 0);

begin
--PORT DECLARATIONS
    ALU: arithmetic_logic_unit port map (
        dataA => busA,
        dataB => busB,
        FS_code => FSel,
        V => V,
        C_out => C,
        dataG => ALU_out
    );

    shifter: shifter_16bit port map (
        input => busB,
        sel0 => FSel(0),
        sel1 => FSel(1),
        sel2 => FSel(2),
        sel3 => FSel(3),
        y => shifter_out
    );

    z_flag: zero_detect_16 port map (
        data => ALU_out,
        z => Z
    );

    muxF: mux2_16bit port map (
        S => FSel(4),
        In0 => ALU_out,
        In1 => shifter_out,
        Z => F
    );

    N <= output(15);
    F <= output;
end Behavioral;

```

## 2.8.2 Function\_unit Test Bench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY function_unit_tb IS
END function_unit_tb;

ARCHITECTURE behavior OF function_unit_tb IS
    COMPONENT function_unit
    PORT ( busA, busB : in  STD_LOGIC_VECTOR (15 downto 0);
          FSel : in  STD_LOGIC_VECTOR (4 downto 0);
          V, C, N, Z : out STD_LOGIC;
          F : out  STD_LOGIC_VECTOR (15 downto 0));
    END COMPONENT;

```



```

--Inputs
signal busA, busB : std_logic_vector(15 downto 0) := (others => '0');
signal FSel : std_logic_vector(4 downto 0) := (others => '0');
--Outputs
signal V, C, N, Z : std_logic;
signal F : std_logic_vector(15 downto 0);

BEGIN
  uut: function_unit PORT MAP (
    busA => busA,
    busB => busB,
    FSel => FSel,
    V => V,
    C => C,
    N => N,
    Z => Z,
    F => F
  );

  stim_proc: process
  begin
    wait for 100 ns;

    --Test arithmetic functions
    busA <= "0000111100000000";
    busB <= "0000000011110000";
    wait for 10 ns;    FSel <= "00000";
    wait for 10 ns;    FSel <= "00001";
    wait for 10 ns;    FSel <= "00010";
    wait for 10 ns;    FSel <= "00011";
    wait for 10 ns;    FSel <= "00100";
    wait for 10 ns;    FSel <= "00101";
    wait for 10 ns;    FSel <= "00110";
    wait for 10 ns;    FSel <= "00111";


    --Test logical functions
    busA <= "0000111100001111";
    busB <= "0000000011111111";
    wait for 10 ns;    FSel <= "01000";
    wait for 10 ns;    FSel <= "01010";
    wait for 10 ns;    FSel <= "01100";
    wait for 10 ns;    FSel <= "01110";

    --Test shifter
    busB <= "0000000000000011";
    wait for 10 ns;    FSel <= "10000";
    wait for 10 ns;    FSel <= "10100";
    wait for 10 ns;    FSel <= "11000";
    wait;
  end process;
END;


```

## 2.8.3 Function\_unit Test Results

### Arithmetic & Logic testing

 

### Shift testing

 

## 3 Datapath

### 3.1 Datapath Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;
```

entity datapath is

```
Port ( data_in, constant_in : in  STD_LOGIC_VECTOR (15 downto 0);
      dest_select, Aselect, Bselect : in  STD_LOGIC_VECTOR (2 downto 0);
      FSelect : in  STD_LOGIC_VECTOR (4 downto 0);
      load_enable, CLK, MBSelect, MDSelect : in  STD_LOGIC;
      data_out, address_out : out STD_LOGIC_VECTOR (15 downto 0);
      V,C,N,Z : out  STD_LOGIC);
```

end datapath;

architecture Behavioral of datapath is

--COMPONENTS

```
    component register_file_v2 is
        port( load_enable, CLK : in  STD_LOGIC;
              dest_select, Asel, Bsel : in  STD_LOGIC_VECTOR(2 downto 0);
              DData : in  STD_LOGIC_VECTOR (15 downto 0);
              AData, BData : out  STD_LOGIC_VECTOR (15 downto 0));
    end component;
```

```
    component function_unit is
        port( busA, busB : in  STD_LOGIC_VECTOR (15 downto 0);
              FSel : in  STD_LOGIC_VECTOR (4 downto 0);
              V, C, N, Z : out  STD_LOGIC;
              F : out  STD_LOGIC_VECTOR (15 downto 0));
    end component;
```

```
    component mux2_16bit is
        port( S: in  STD_LOGIC;
              In0, In1: in  STD_LOGIC_VECTOR (15 downto 0);
```

```

        Z: out STD_LOGIC_VECTOR (15 downto 0)
    );
end component;

--SIGNALS
signal Bdata, FData, ABus, BBus, MuxDData: STD_LOGIC_VECTOR (15 downto 0);

begin
--PORT MAPS
    regFile: register_file_v2 port map (
        load_enable => load_enable,
        CLK => CLK,
        dest_select => dest_select,
        Aselect => Aselect,
        Bselect => Bselect,
        DData => MuxDData,
        AData => ABus,
        BData => Bdata
    );

    functUnit: function_unit port map (
        busA => ABus,
        busB => BBus,
        FSel => FSelect,
        V => V,
        C => C,
        N => N,
        Z => Z,
        F => FData
    );

    muxB: mux2_16bit port map (
        S => MBSelect,
        In0 => Bdata,
        In1 => constant_in,
        Z => BBus
    );

    muxD: mux2_16bit port map (
        S => MDSelect,
        In0 => FData,
        In1 => data_in,
        Z => MuxDData
    );

    data_out <= BBus;
    address_out <= ABus;
end Behavioral;

```

### 3.2 Datapath Test Bench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.numeric_std.all;

```

```

ENTITY datapath_tb IS
END datapath_tb;

```

ARCHITECTURE behavior OF datapath\_tb IS

COMPONENT datapath

```
PORT(
    data_in, constant_in : in  STD_LOGIC_VECTOR (15 downto 0);
    dest_select, Aselect, Bselect : in  STD_LOGIC_VECTOR (2 downto 0);
    FSelect : in  STD_LOGIC_VECTOR (4 downto 0);
    load_enable, CLK, MBSelect, MDSelect : in  STD_LOGIC;
    data_out, address_out : out STD_LOGIC_VECTOR (15 downto 0);
    V,C,N,Z : out  STD_LOGIC);
END COMPONENT;
```

--Inputs

```
signal data_in, constant_in : std_logic_vector(15 downto 0) := (others => '0');
signal dest_select, Aselect, Bselect : std_logic_vector(2 downto 0) := (others => '0');
signal FSelect : std_logic_vector(4 downto 0) := (others => '0');
signal load_enable, CLK, MBSelect, MDSelect : std_logic := '0';
```

--Outputs

```
signal data_out, address_out : std_logic_vector(15 downto 0);
signal V,C,N,Z : std_logic;
```

constant CLK\_period : time := 10 ns;

BEGIN

```
uut: datapath PORT MAP (
    data_in => data_in,
    constant_in => constant_in,
    dest_select => dest_select,
    Aselect => Aselect,
    Bselect => Bselect,
    FSelect => FSelect,
    load_enable => load_enable,
    CLK => CLK,
    MBSelect => MBSelect,
    MDSelect => MDSelect,
    data_out => data_out,
    address_out => address_out,
    V => V,
    C => C,
    N => N,
    Z => Z
);
```

CLK\_process : process

begin

```
    CLK <= '0';
    wait for CLK_period/2;
    CLK <= '1';
    wait for CLK_period/2;
```

end process;

stim\_proc: process

begin

wait for 100 ns;

--ALU TEST DESCRIPTION:

```
-- This test loads the value "0000111100000000" into every register. This value is read from
-- register 4 into the function unit (through data line A. Each function is tested and the result
-- stored into register 5. The contents of register 4 can be read on address_out. When
```

-- MBSelct is set to '1', register 5 can be read on data\_out.

--Set Registers

```
MDSelect <= '1';
data_in <= "0000111100000000";
dest_select <= "000";
load_enable <= '1';
```

for i in 0 to 7 loop

wait for CLK\_period\*2;

dest\_select <= STD\_LOGIC\_VECTOR (unsigned(dest\_select) + 1);

end loop;

--Test ALU functionality as described above

```
MBSelct <= '1';
MDSelect <= '0';
dest_select <= "101";
Aselect <= "100";
Bselect <= "101";
constant_in <= "1111000000000000";
```

```
MBSelct <= '1';
load_enable <= '1';          wait for 10 ns;
FSelect <= "00000";          -- A
load_enable <= '0';
MBSelct <= '0'; wait for 20 ns;
```

```
MBSelct <= '1';
load_enable <= '1';          wait for 10 ns;
FSelect <= "00001";          -- A + 1
load_enable <= '0';
MBSelct <= '0'; wait for 20 ns;
```

```
MBSelct <= '1';
load_enable <= '1';          wait for 10 ns;
FSelect <= "00011";          -- A + constant + 1
load_enable <= '0';
MBSelct <= '0'; wait for 20 ns;
```

```
MBSelct <= '1';
load_enable <= '1';          wait for 10 ns;
FSelect <= "00110";          -- A - 1
load_enable <= '0';
MBSelct <= '0'; wait for 20 ns;
```

```
MBSelct <= '1';
load_enable <= '1';          wait for 10 ns;
FSelect <= "01000";          -- A and constant
load_enable <= '0';
MBSelct <= '0'; wait for 20 ns;
```

```
MBSelct <= '1';
load_enable <= '1';          wait for 10 ns;
FSelect <= "01100";          -- A xor constant
load_enable <= '0';
MBSelct <= '0'; wait for 20 ns;
```

```

MBSelect <= '1';
load_enable <= '1';          wait for 10 ns;
FSelect <= "01110";          -- not A
load_enable <= '0';
MBSelect <= '0'; wait for 20 ns;

```

#### --SHIFT TEST DESCRIPTION:

```

-- This test loads "0000000000000011" into register 4. This value is read from here into the
-- function unit (through data line B. The value is shifted and stored back into register 2.
-- The contents of register 2 can be read on address_out.

```

#### --Set Register 4

```

load_enable <= '0';
MDSelect <= '1';
data_in <= "0000000000000011";
dest_select <= "100";
load_enable <= '1';          wait for 10 ns;

```

```

load_enable <= '0';
MDSelect <= '0';
MBSelect <= '0';
Aselect <= "010";
Bselect <= "100";
FSelect <= "11000";

```

for i in 0 to 15 loop

```

        load_enable <= '1';          wait for 10 ns;
        load_enable <= '0';          wait for 20 ns;

```

end loop;

```


wait;
end process;

```

END;

## 3.3 Datapath Test Results

### ALU functionality

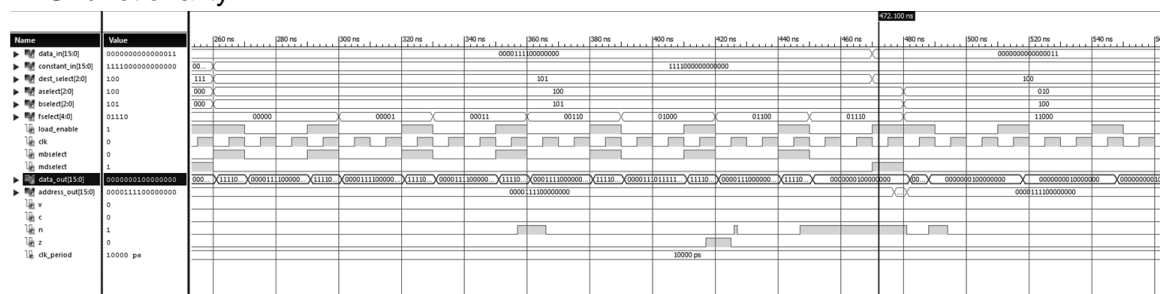

### Shifter Functionality

